


Topic 15: Modular sequential logic: registers

Thursday, January 31, 2019 4:45 PM


I. Registers

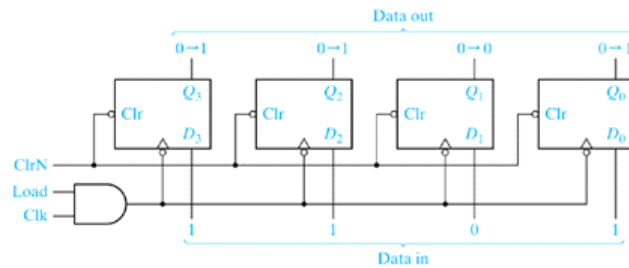1. **Definition:** a synchronous sequential circuit that will store and move n-bit data, either serially or in parallel, in n flip-flops


e.g. 4-bit D flip-flop with clear, load and clock inputs



(a) Using gated clock

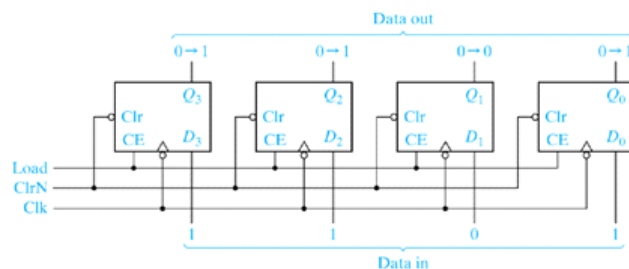

(b) With clock enable

 


(c) Symbol

© Cengage Learning 2014

II. Shift registers

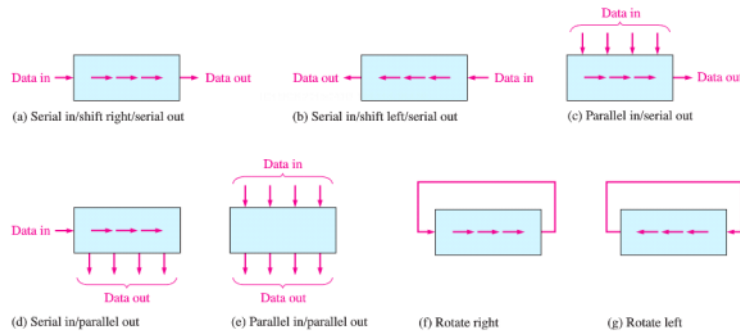
1. **SRGn:** n-bit shift register. e.g. SRG4 indicates a 4-bit shift register
2. **Type of shift register:**
 - a. **Serial shifting:** movement of data from one end of a shift register to the other at a rate of one bit per clock pulse
 - b. **Parallel shifting:** movement of data into all flip-flops of a shift register at the same time
 - c. **Rotation:** in serial shift register, the output of the last FF is connected back to the synchronous input of the first FF. This results in continuous circulation of the same data
 - d. Right shift, left shift, bidirectional shift register
 - e. **Parallel-load shift register:** a shift register that can be preset to any value by directly loading a binary number into its internal flip-flops
 - f. **Universal shift register:** a shift register that can operate with any combination of serial and parallel inputs and outputs

e.g. serial in/serial out, serial in/parallel out, parallel in/serial out, parallel in/parallel out, and bidirectional operation




3. Serial in/serial out shift register

- Symbol of a serial in/serial out SRG8

 


Commercial product: SN7491A -- 8-bit serial-in, serial-out shift register

 - Diagram of a 4-bit serial in/serial out shift register:



 Q1: Given the Clock and data waveforms, draw the output waveforms of each flip-flop (Q0 - Q3)



Now thinking we have a series of data (1010) to store: start from the LSB

TABLE 8-1

Shifting a 4-bit code into the shift register in Figure 8-3. Data bits are indicated by a beige screen.

CLK	FF0 (Q_0)	FF1 (Q_1)	FF2 (Q_2)	FF3 (Q_3)
Initial	0	0	0	0
1	0	0	0	0
2	1	0	0	0
3	0	1	0	0
4	1	0	1	0

To read the data out, another 4 clock pulse is needed

TABLE 8-2

Shifting a 4-bit code out of the shift register in Figure 8-3. Data bits are indicated by a beige screen.

CLK	FF0 (Q_0)	FF1 (Q_1)	FF2 (Q_2)	FF3 (Q_3)
Initial	1	0	1	0

Readout


Data bits are indicated by a beige screen.

CLK	FF0 (Q_0)	FF1 (Q_1)	FF2 (Q_2)	FF3 (Q_3)
Initial	1	0	1	0
5	0	1	0	1
6	0	0	1	0
7	0	0	0	1
8	0	0	0	0

Readout.

 Q2: in the following 5-bit serial in/serial out shift register (SGR5), a series of data (01011) is going to be stored (the rightmost bit goes in first).

- What data is stored in the output of each flip-flop (from Q_0 to Q_4) after 4 clock cycles?
- If the data input is fixed to logic 1 after the 5-bit data all go into the register, what data is stored in the output of each flip-flop (from Q_0 to Q_4) after 7 clock cycle?



4. Serial in/parallel out shift register

*n clk cycle to store
1 clk cycle to read*


 
 


FIGURE 8-6 A serial in/parallel out shift register.

The store process is the same as serial in/serial out shift register

Commercial product: SN74164 -- 8-bit serial-in, serial/parallel -out shift register;
SN796 -- 5-bit serial-in, serial-parallel - out shift register with asynchronous common clear and preset



5. Parallel in/serial out shift register

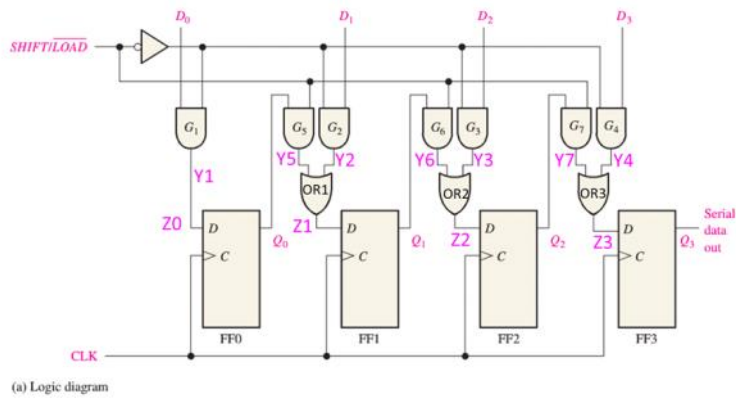

Q3: If $\text{SHIFT}/\overline{\text{LOAD}} = 0$, what are the outputs of the AND gates Y1~Y7? What are the outputs of the OR gates Z1~Z3? When a clock rising edge is coming, what are the outputs of the flip-flops Q0~Q3? Do you think the registers are doing loading or shifting function?


Q4: If $\text{SHIFT}/\overline{\text{LOAD}} = 1$, what are the outputs of the AND gates Y1~Y7? What are the outputs of the OR gates Z1~Z3? When a clock rising edge is coming, what are the outputs of the flip-flops Q0~Q3? Do you think the registers are doing loading or shifting function?

 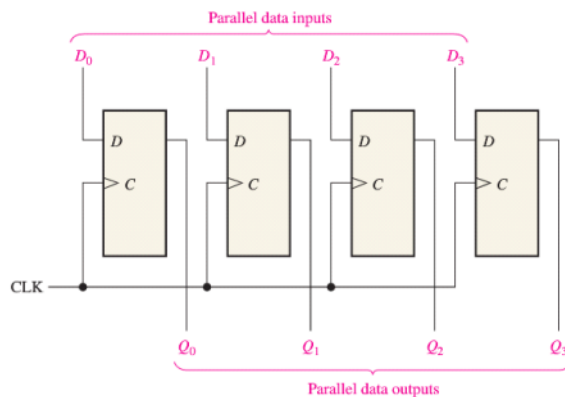6. Parallel in/parallel out shift register




The 74HC195 4-bit parallel access shift register.

7. Bidirectional shift register

 


 Q5: Determine the state of the bidirectional shift register after each clock pulse for the given control input waveform. Assume that $Q_0=1, Q_1=1, Q_2=0, Q_3=1$ and the serial data input is LOW.



Commercial product: SN74164 -- 4-bit bidirectional serial-in, parallel-out shift register

 8. Universal register -- 74HC194 4-bit universal shift register



Q6: Design a 4-bit SRG with control input SH (Shift) and L (Load) using D flip-flops. If both SH and L are 0, the stored data in the SRG will not change; if L is 1, the SRG will do parallel loading from data input I3~I0; if SH is 1 and L is 0, the SRG should shift to the right.

a. Complete the state table

L	SH	Q_3^*	Q_2^*	Q_1^*	Q_0^*
0	0	Q_3	Q_2	Q_1	Q_0
1	X	I_3	I_2	I_1	I_0
0	1	0	Q_3	Q_2	Q_1

b. Generate the Boolean function for D3~D0

$$D_3 = L' SH' Q_3 + L I_3$$

$$D_2 = L' SH' Q_2 + L I_2 + L' SH Q_3$$

$$D_1 = L' SH' Q_1 + L I_1 + L' SH Q_2$$

$$D_0 = L' SH' Q_0 + L I_0 + L' SH Q_1$$

(Input circuit for FFs)

$$D = Q^*$$

$$Y = \overline{S} D_0 + S D_1$$

$$\begin{aligned} D_3 &= L'SH'Q_3 + LI_3 \\ D_2 &= L'SH'Q_2 + LI_2 + L'SH'Q_3 \\ D_1 &= L'SH'Q_1 + LI_1 + L'SH'Q_2 \\ D_0 &= L'SH'Q_0 + LI_0 + L'SH'Q_1 \end{aligned}$$

III. Shift register counter

- **Counter:** a sequential circuit that has a number of binary outputs whose states progress through a fixed sequence, either ascending or descending or even nonlinear. **A counter goes back to its initial state after counting the last state.**

e.g. 0, 1, 2, 3, 0, 1, 2, 3 ...
3, 2, 1, 0, 3, 2, 1, 0...
1, 3, 5, 7, 1, 3, 5, 7....

- **Type I: Ring counter**

Definition: a shift register with the serial output connected back to the serial input to produce special sequence

e.g. **10-bit ring counter**

 


TABLE 8-5
Ten-bit ring counter sequence.

Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	0	0	0	0
3	0	0	0	1	0	0	0	0	0	0
4	0	0	0	0	1	0	0	0	0	0
5	0	0	0	0	0	1	0	0	0	0
6	0	0	0	0	0	0	1	0	0	0
7	0	0	0	0	0	0	0	1	0	0
8	0	0	0	0	0	0	0	0	1	0
9	0	0	0	0	0	0	0	0	0	1

10-bit RC
10 state

FFs.
↑
20-bit RC
↑
20 state


Q7: If a 10 bit ring counter has an initial state Q₀:Q₉ = 1 010 000 000 determine the count sequence for the Q outputs for the 1st 10 clock cycles.



Initial state:
Q₀: c10 → c1.
Q₁: c11 → c2.
Q₂: c12 → c3.

Q₉: c19 → c10.
c9 → c0.

 Q8: What is the initial state of the 10-bit ring counter if the output Q₉ show the following waveform




• **Type II: Johnson counter**

The complement of the output of the last FF is connected back to the D input of the first FF.

A n-bit (n-FFs) Johnson counter can realize modulus-2n counter

e.g. **4-bit Johnson counter**

4-bit Johnson → 8 state

 

Q ₀	Q ₁	Q ₂	Q ₃
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1

4-bit Johnson counter → 8 states mod 8.


3-bit → 6 state.

Q ₀	Q ₁	Q ₂
0	0	0
1	0	0
1	1	0
1	1	1
0	1	1
0	0	1
0	0	0

n-bit → mod 2n.

n-bit → 2n state

↓
n-FFs.

 

8 of states.

Q9: How many flip-flops are required to implement a:

- Modulus-6 Ring Counter** 6 FFs.
- Modulus-10 Johnson Counter** 5 FFs.
- Modulus-14 Ring Counter**
- Modulus-16 Johnson Counter**
- Modulus-6 Binary Counter**